

# **8-bit Shift Register**

---

**Project Report**

**Submitted To:**

**Dr. Awais M. Kamboh**

**Submitted By:**

**Haris Suhail**


**Uzair Akbar**

**Moez Akmal**

**Dated : May 23, 2016**

## DELIVERABLES:


### Schematic of DFFR cells:

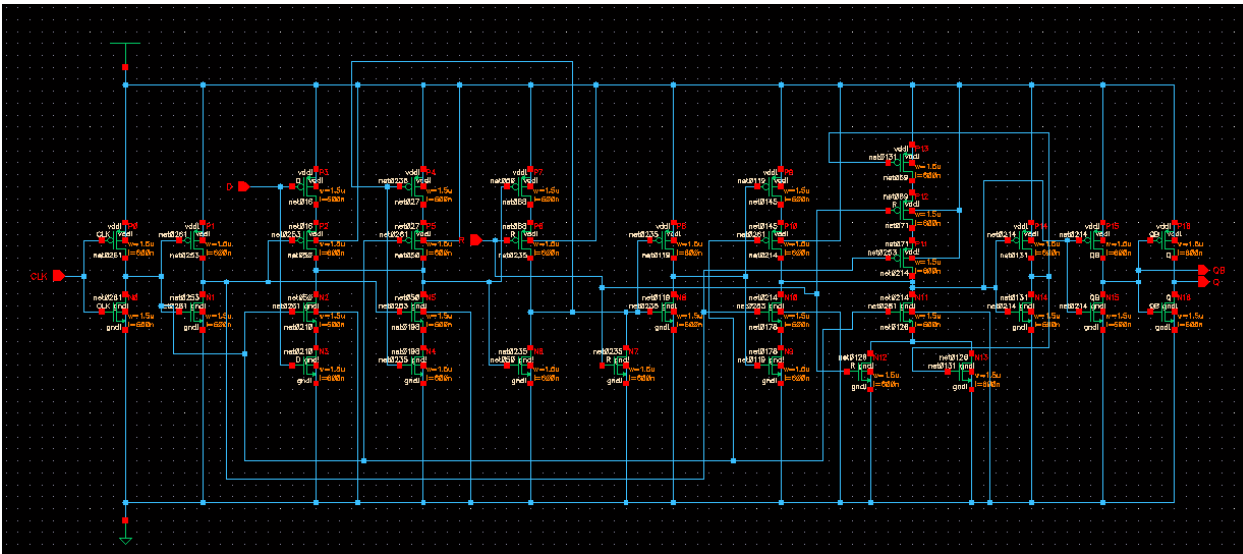


### Post Layout Simulation:

#### Timing Delays:

 
#### Propagation Delay Low to High ( $t_{pLH}=1.578\text{ns}$ )




Propagation Delay (tpHL 1.7621ns)

 

Setup time for Rising edge(589.4ps)

 

Setup time for falling edge(735.3ps)

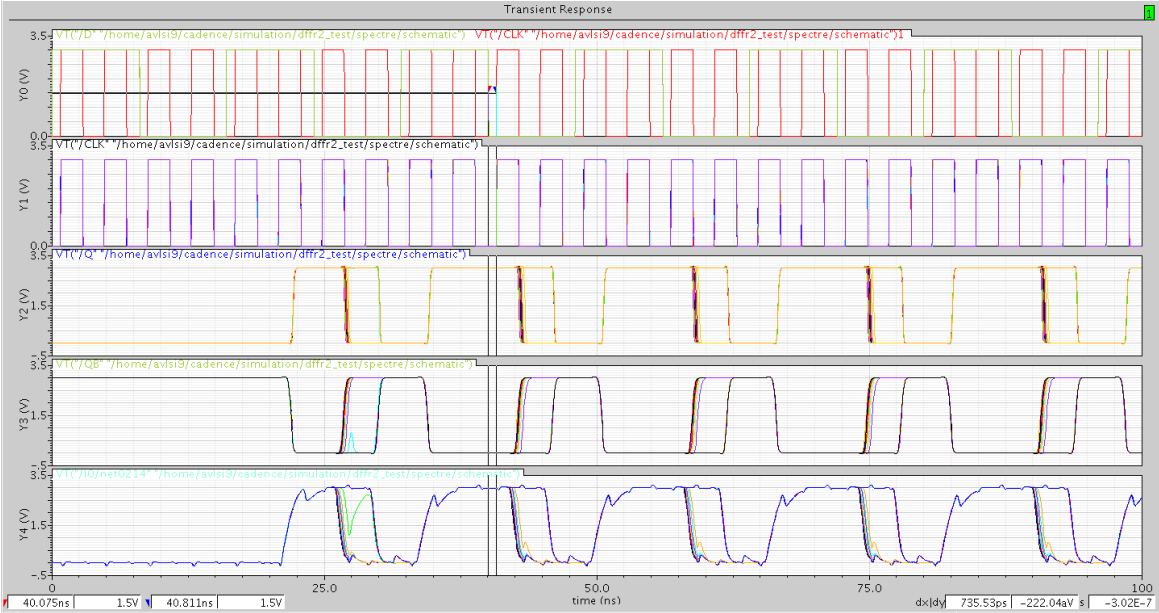

LVS RESULTS OF DFFR:

```

$ (#) $CDS: LVS.exe version 5.1.0 06/20/2007 02:10 (cicln03) $
Command line: /usr/Cadence/tools.lnx86/diff/bin/32bit/LVS.exe -dir /home/avlsi9/Group9_n/LVS -l -s -t /home/avlsi9/Group9_n/L
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.

Net-list summary for /home/avlsi9/Group9_n/LVS/layout/netlist
count
24      nets
7       terminals
17      pmos
17      rmos

Net-list summary for /home/avlsi9/Group9_n/LVS/schematic/netlist
count
24      nets
7       terminals
17      pmos
17      rmos

Terminal correspondence points
N17      N16      CLK
N13      N11      D
N12      N9       Q
N23      N25      QB
N9       N8       R
N16      N1       gnd!
N0       N0       vdd!


Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
nfet pfet rmos4 pmos4 cap

The net-lists match.


          layout schematic
un-matched instances
rewired    0      0
size errors 0      0
pruned     0      0
active     34     34
total      34     34

```

## SCHEMATICS OF 4X1 MUX:

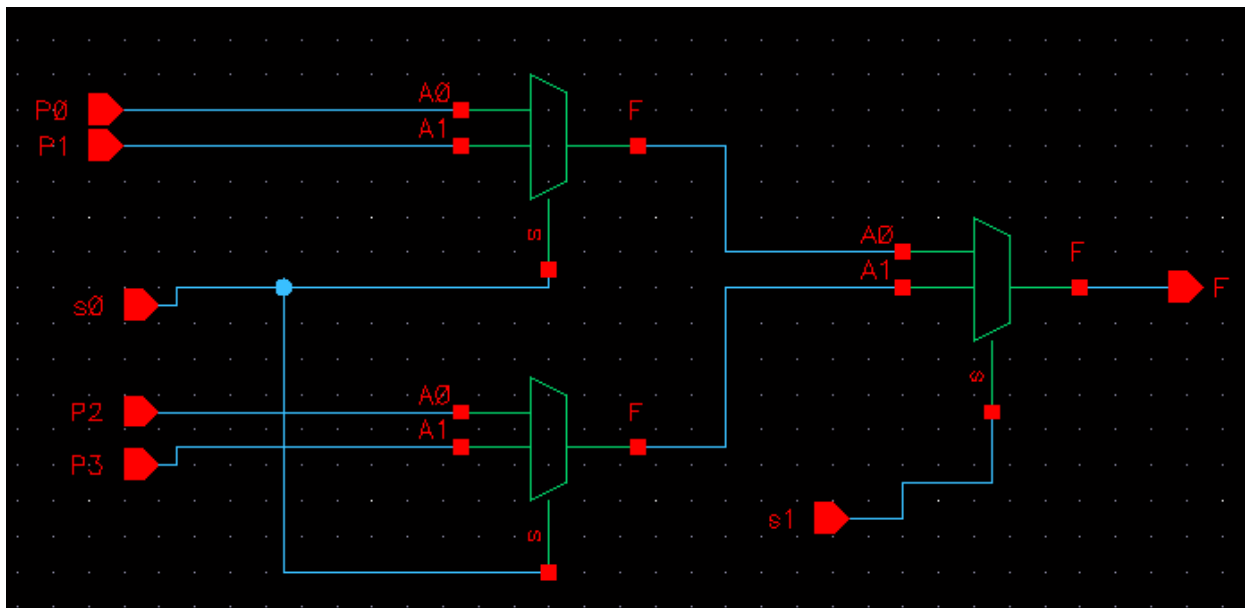

## LAYOUT OF 4X1 MUX:

 

# LVS OF 4X1 MUX:

```
@(#)$CDS: LVS.exe version 5.1.0 06/20/2007 02:10 (cicln03) $

Command line: /usr/Cadence/tools.lnx06/dftII/bin/32bit/LVS.exe -dir /home/avlsi9/Group9_n/LVS -l -s -t /home/avlsi9/Group9_n/LVS/layout /home/avlsi9/Group9_n/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.

Net-list summary for /home/avlsi9/Group9_n/LVS/layout/netlist
count
14      nets
9       terminals
9       pmos
9       rmos

Net-list summary for /home/avlsi9/Group9_n/LVS/schematic/netlist
count
14      nets
9       terminals
9       pmos
9       rmos


Terminal correspondence points
M1      M4      F
M13     N9      P0
M11     N3      P1
N0      N2      P2
N6      N8      P3
M4      N1      gnd!
N7      N7      s0
M5      N6      s1
N2      N0      vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
nfet pfet rmos4 pmos4 cap


The net-lists match.

          layout schematic
un-matched      0      0
revired         0      0
size errors     0      0
pruned          0      0
```

# SCHEMATICS OF 8 BIT SHIFT REGISTER:

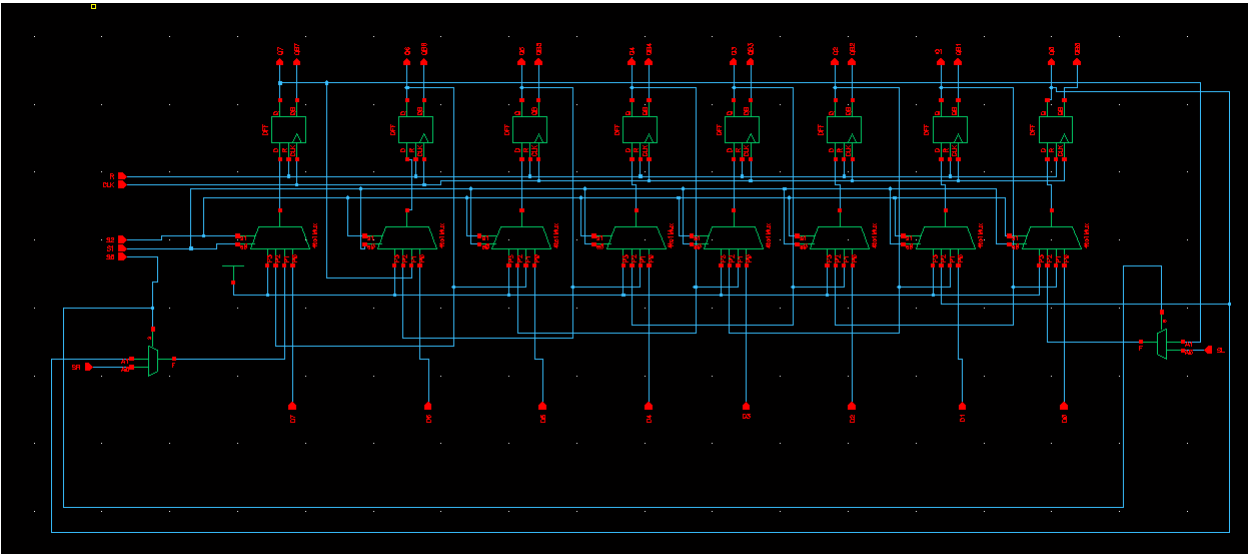

# LAYOUT OF 8 BIT SHIFT REGISTER:

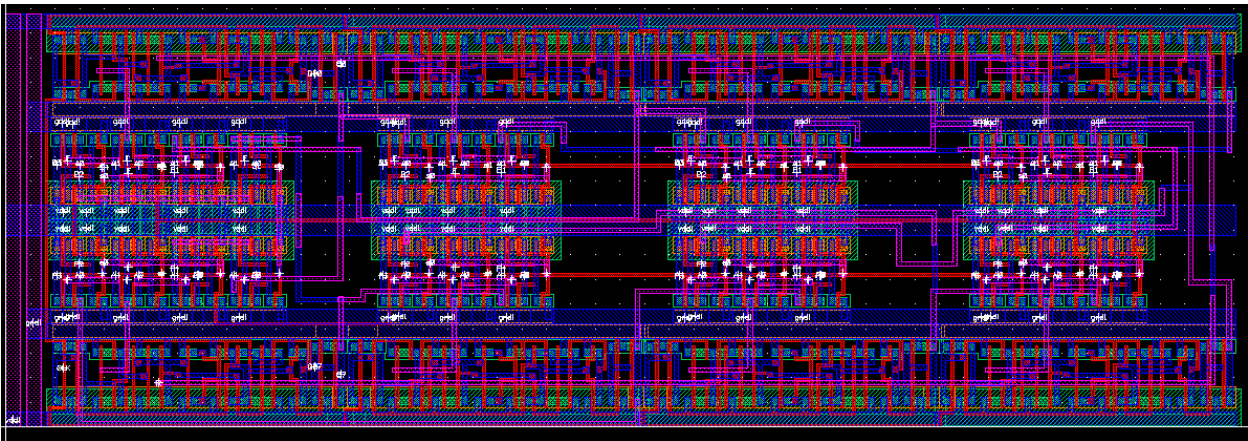

# LVS OF 8 BIT SHIFT REGISTER:

```
[s(#)$CDS: LVS.exe version 5.1.0 06/20/2007 02:10 (cicln03) $

Command line: /usr/Cadence/tools.lnx86/diII/bin/32bit/LVS.exe -dir /home/avlsi9/Group9_n/LVS -l -s -t /home/avlsi9/Group9_n/LVS/layout /home/avlsi9/Group9_n/LVS/schemat
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.

Net-list summary for /home/avlsi9/Group9_n/LVS/layout/netlist
count
221      nets
33       terminals
214      pmos
214      rmos

Net-list summary for /home/avlsi9/Group9_n/LVS/schematic/netlist
count
221      nets
33       terminals
214      pmos
214      rmos

Terminal correspondence points
N131    N19    CLK
N206    N33    D0
N72     N15    D1
N93     N30    D2
N2      N2      D3
N86     N23    D4
N67     N9     D5
N9      N12    D6
N186    N20    D7
N114    N42    Q0
N43     N26    Q1
N180    N13    Q2
N71     N17    Q3
N146    N27    Q4
N70     N14    Q5
N66     N8     Q6
N167    N4     Q7
N217    N43    QB0
N122    N6     QB1
N148    N28    QB2
N7      N11    QB3
N41     N24    QB4
N75     N18    QB5
N171    N5     QB6
N159    N38    QB7
N50     N32    R
N107    N37    S0
N149    N34    S1
N88     N25    S2
N136    N21    SL
N62     N7     SR
N28     N1     gnd!
N1      N0     vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
nfet pfet rmos4 pmos4 cap

The net-lists match

          layout schematic
instances
un-matched 0 0
revied     0 0
size errors 0 0
pruned     0 0
active     428 428
total      428 428

          nets
un-matched 0 0
merged     0 0
pruned     0 0
active     221 221
total      221 221


          terminals
un-matched 0 0
matched but different type 0 0
total      33 33

Probe files from /home/avlsi9/Group9_n/LVS/schematic
devbad.out:
```


## Truth Table for Shift Register:

| S2 | S1 | S0 | Function  | Delay (ns) |
|----|----|----|---|------------|
| 0  | 0  | X  | Parallel Load                                       | 2.489      |
| 0  | 1  | 0  | Shift Right   | 2.5185     |
| 0  | 1  | 1  | Rotate Right  | 2.7024     |
| 1  | 0  | 0  | Shift Left  | 2.412      |
| 1  | 0  | 1  | Rotate Left   | 2.7231     |
| 1  | 1  | X  | Set (data output bit go to 1)                       | 2.532      |
| X  | X  | X  | Reset (When Reset =1, all data output goes to zero) |            |

## Delay for State 000:

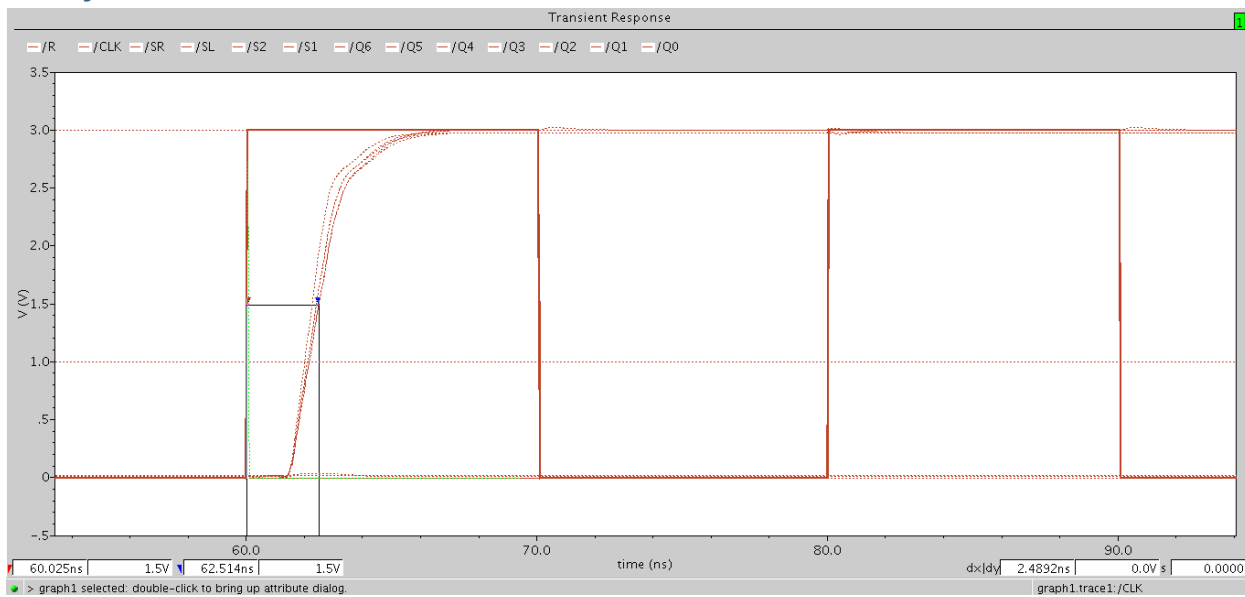


## Delay for State 010:

 





# Delay for State 011:

 


# Delay for State 100:

 

# Delay for State 101:

 


# Delay for State 110:

 


## POWER MEASUREMENT:


### Static Power:

 


### Transient Power/ Dynamic Power:

 

## Average Power :(2.8369 E-4)

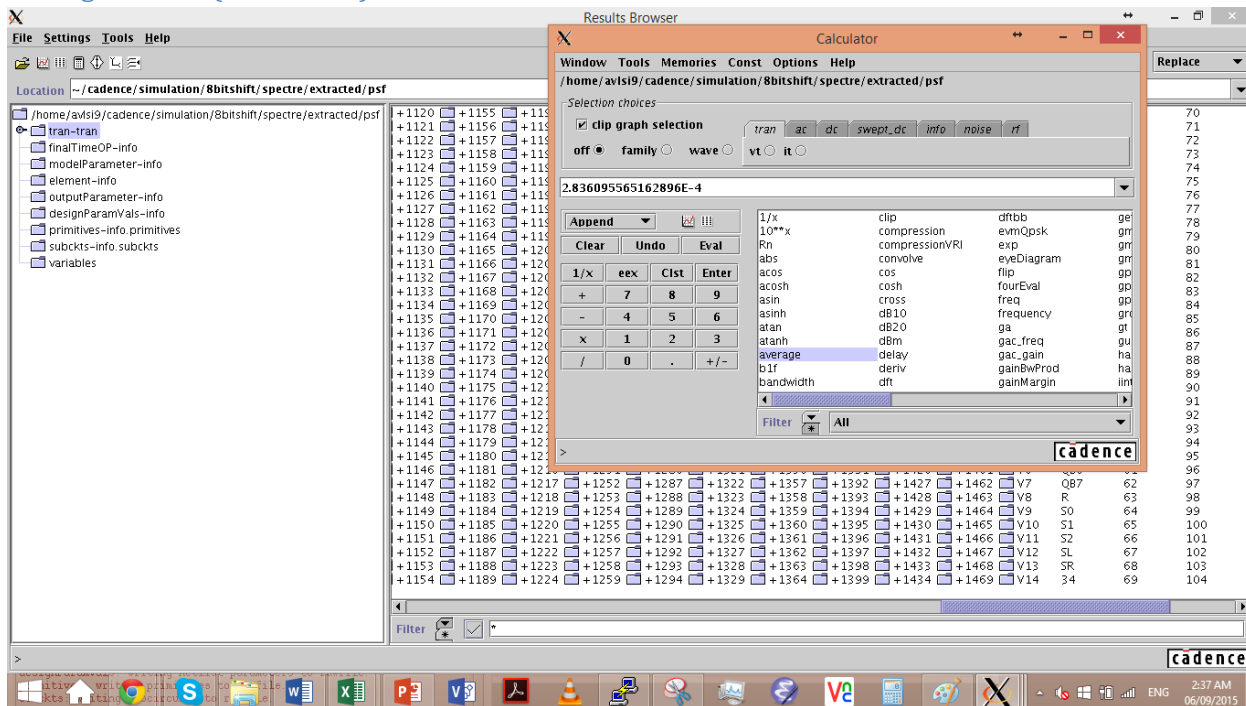


## Peak Power: (0.0124)

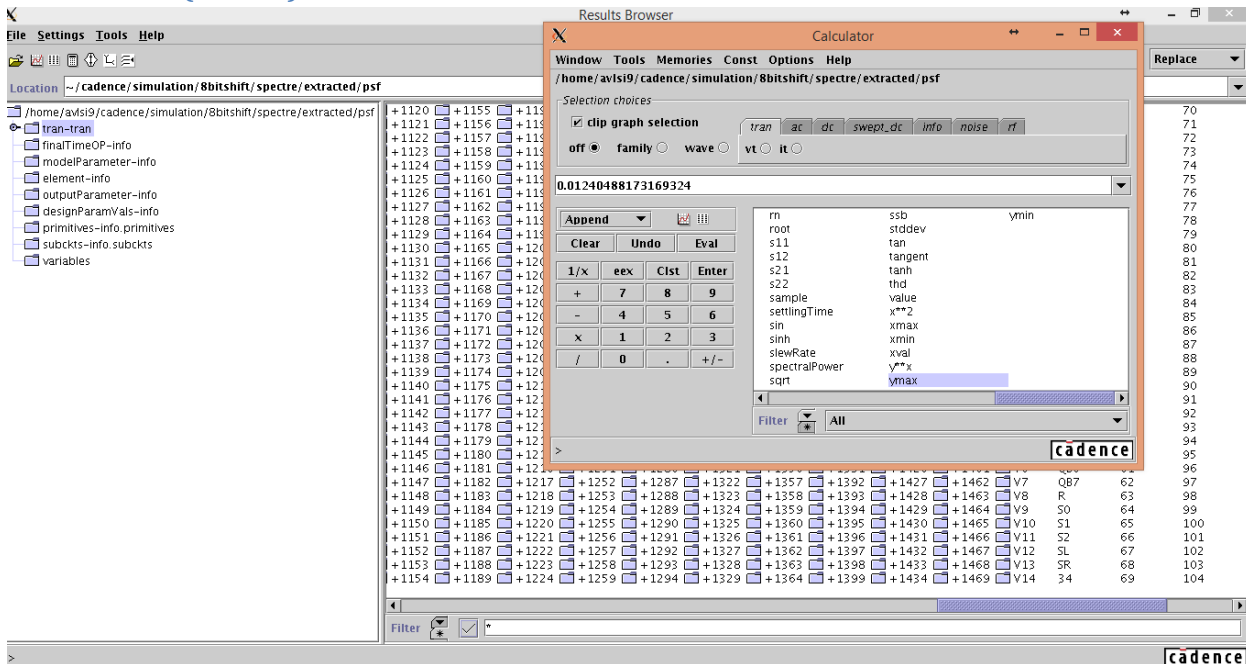
 
# Energy Consumption:


For  $T=0 \rightarrow 1.5\mu s \Rightarrow 4.25414E-10$

The screenshot shows the Cadence Results Browser window with a list of simulation results. A Calculator window is open, displaying the result  $4.254143347744349E-10$ . The calculator also shows the signal `Signal[getData("pwr" ?result "tran-tran")]` and the definite integral settings: Initial Value 0, Final Value 1.5u.




# Extra Credit:


## SCHEMATICS OF COUNTER:

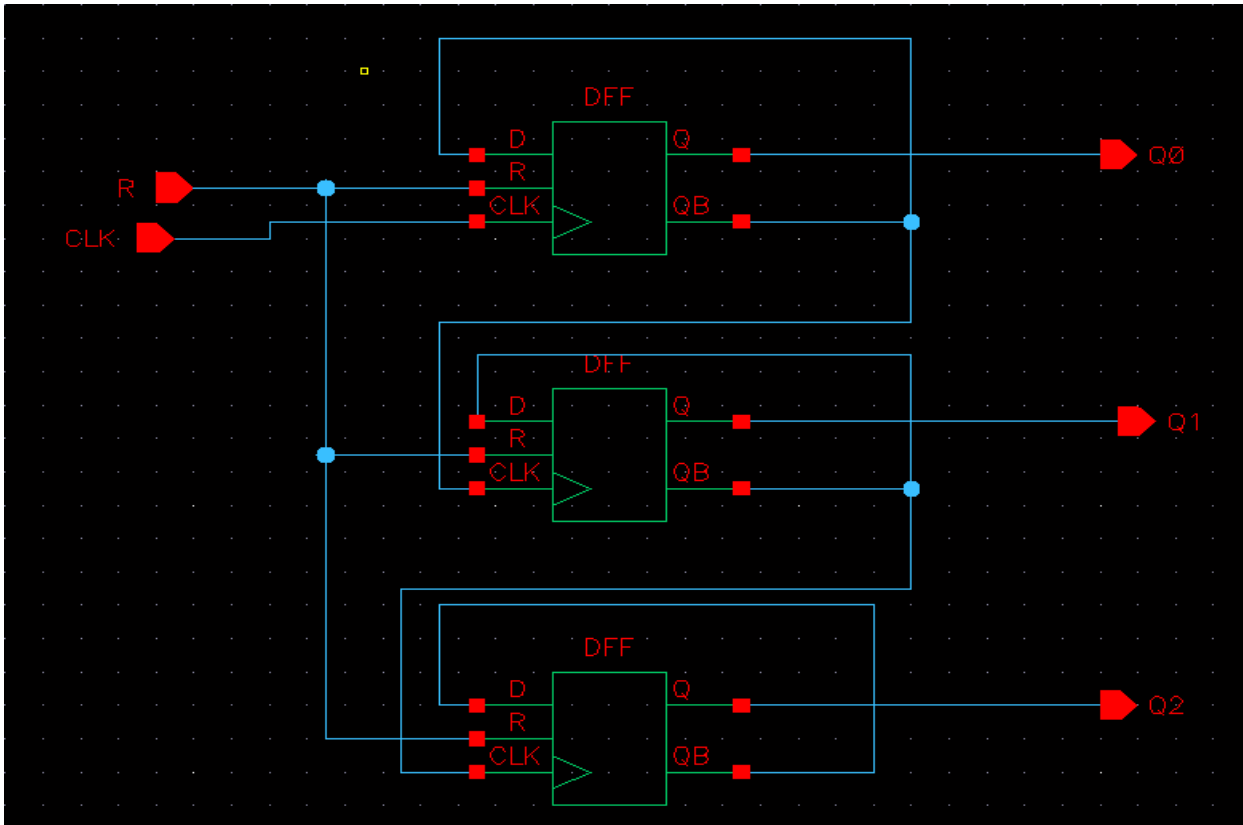


## SIMULATION RESULTS OF COUNTER:

 


## SCHEMATICS OF 2X1 MUX:

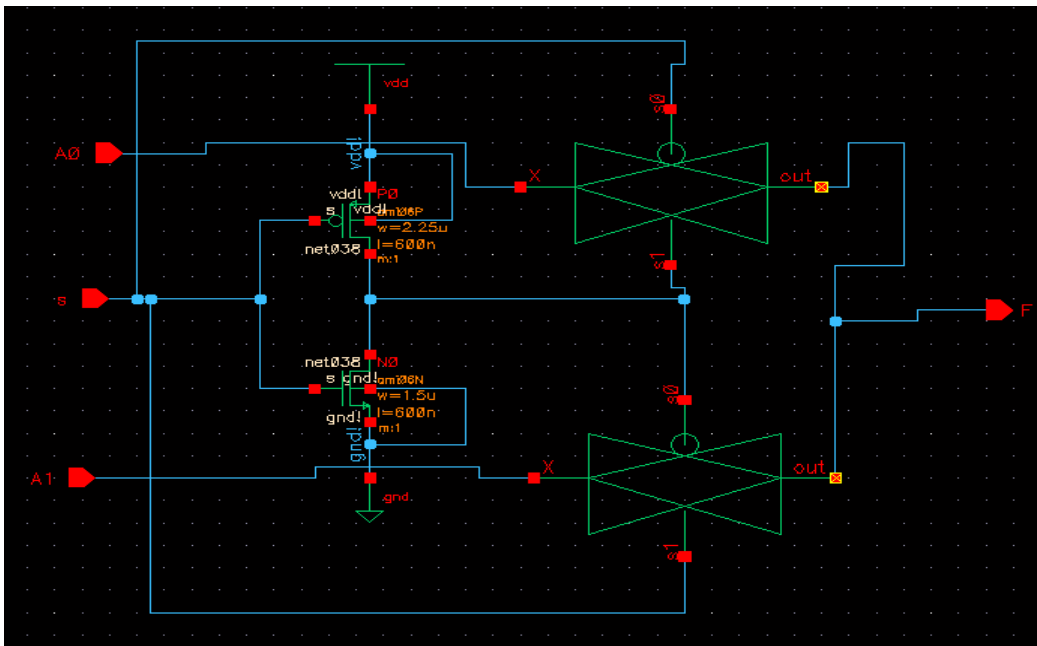


## SYMBOL OF 2X1 MUX:

 

# Simulation of Schematics of MUX 2x1:

 

 
# Post Layout (Extracted) Simulation of MUX 2x1:





## LAYOUT OF 2X1 MUX:

 

Widths of NMOS = 1.500

Widths of PMOS = 2.250

## LVS OF 2X1 MUX:

```
@(#)$CDS: LVS.exe version 5.1.0 06/20/2007 02:10 (cicln03) $
Command line: /usr/Cadence/tools.lnx86/dfII/bin/32bit/LVS.exe -dir /home/avlsi9/Group9_n/LVS -l -s -t /home/avlsi9/Group9_n/LVS/layout /home/avlsi9/Group9_n/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.

Net-list summary for /home/avlsi9/Group9_n/LVS/layout/netlist
count
7          nets
6          terminals
3          pmos
3          rmos

Net-list summary for /home/avlsi9/Group9_n/LVS/schematic/netlist
count
7          nets
6          terminals
3          pmos
3          rmos

Terminal correspondence points
N6      N8      A0
N5      N6      A1
N0      N2      F
N2      N1      gnd!
N3      N4      s
N1      N0      vdd!

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
nfet pfet rmos4 pmos4 cap

The net-lists match.

layout schematic
```

## LVS OF Transmission Gate:

```
@(#)$CDS: LVS.exe version 5.1.0 06/20/2007 02:10 (cicln03) $
Command line: /usr/Cadence/tools.lnx86/dfII/bin/32bit/LVS.exe -dir /home/avlsi9/Group9_n/LVS -l -s -t /home/avlsi9/Group9_n/LVS/layout /home/avlsi9/Group9_n/LVS/schematic
Like matching is enabled.
Net swapping is enabled.
Using terminal names as correspondence points.

Net-list summary for /home/avlsi9/Group9_n/LVS/layout/netlist
count
6          nets
4          terminals
1          pmos
1          rmos

Net-list summary for /home/avlsi9/Group9_n/LVS/schematic/netlist
count
6          nets
6          terminals
1          pmos
1          rmos

Terminal correspondence points
N2      N6      X
N5      N7      out
N3      N5      s0
N1      N4      s1

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
nfet pfet rmos4 pmos4 cap

The net-lists match.

layout schematic
instances
un-matched      0      0
rewired          0      0
size errors      0      0
pruned           0      0
active           2      2
total            2      2

nets
un-matched      0      0
```

# Discussion Topics:

**Q1.) Is the DFFR a positive-edge-triggered or negative-edge-triggered FF? Briefly describe the hold time for a d-type flip flop and estimate its value.**

The DFFR that was used in LAB was positive edge triggered. Hold time is the time after the clock edge has occurred for which the data on register input must not change. Mux based DFFR has zero hold time. In Mux based DFFR, the input D on MUX based negative latch doesn't change when positive clock edge has occurred. i.e. the first mux is holding the value. Thus no hold time exists.

**Q2.) Briefly define two of the rules for multi-cell layouts that you feel are most important.**

1. VDD and ground are used in a fashion that they are common for two rows. To accomplish this, we can label each VDD and ground individually and join these using virtual connections. In this way single rail is not needed in cells.
2. It is preferable to have VDD/ground within a cell physically joined together. This requires the knowledge of high level hierarchy.

**Q3.) Briefly discuss the worst-case function of the shift register. Is it what you expected? Why or why not?**

Worst case function of shift register is rotate left/right. This is same as what we expected because the values require the longest path for rotation in any of rotate operation whether left or right.

**Q4.) Briefly discuss the pros and cons of the asynchronous counter versus a synchronous counter.**

- Asynchronous counter: Asynchronous counter is a serial counter i.e. the input signal is applied to the clock input of the first FF, and the output of each FF is connected directly to the clock input of the next.
- Synchronous counter: Synchronous counters are parallel counters since all flip-flops are controlled by a common clock. Logic gates between each stage of the circuit control dataflow from stage to stage so that the desired count behaviour is realized.

The pros and cons are as shown in the table:

|                                    | Asynchronous   | Synchronous   |
|------------------------------------|--|---|
| <b>Circuit</b>                     | The logic circuit of this type of counters is simple to design and we feed output of one FF to clock of next FF                                    | The circuit diagram for type of counter becomes difficult as number of states increase in the counter |
| <b>Propagation Time</b>            | Propagation time delay of this type of counter is :<br><br>$T_p = N * (\text{Delay of 1 FF})$<br><br>which is quite high<br><br>N is number of FFs | Propagation time delay of this type of counter is:<br><br>$T_p = (\text{Delay of 1 FF})$              |
| <b>Maximum operating frequency</b> | And hence operating frequency is Low   | And hence operating frequency is Higher   |

**Q5.) A 2:1 MUX could be implemented with 2 AND logic gates and 1 NOR logic gate. How many transistors would this require for a CMOS implementation? Compare this to the number of transistors required for the transmission gate implementation.**

Single AND/OR gate is implemented by six transistors. Thus a mux requires 2 AND gates, one OR gate and one NOT gate. Which makes a total of 20 transistor. For CMOS implementation we need 4 transistor of Pull Up logic and 4 resistor for pull down and 2 for not gate. Thus for CMOS implementation a total of 10transistors are required. While when using transmission gate, total of 6 transistors are required. ( 4 for transmission gate, 2 for NOT gate).

**Q6.) What layout widths (as defined in Lab 2) did you achieve for the MUX21?**

In 2 to 1 MUX the acquired width in design is 12um. While PMOS width is 2.25um and NMOS width is 1.5um